

# **PNS School of Engineering & Technology**

Nishamani Vihar, Marshaghai, Kendrapara

**Internal Assessment Examination-2022(5th Semester)**

**Subject : Th-5 -Power Electronics & PLC**

**Branch : Electrical & ETC Engineering**

Time :  $1\frac{1}{2}$  Hours

F.M. : 20

1. Answer the following questions(any Five) . [2 x 5]
  - (a) Define latching current.
  - (b) What is  $\frac{dv}{dt}$  triggering of an SCR ?
  - (c) State delay time.
  - (d) Define snubber circuit.
  - (e) What is phase angle in converter ?
  - (f) What is chopper ?
  - (g) What do you mean by duty cycle ?
  
2. Answer the following questions. (any Two) [5 x 2]
  - (a) Explain the construction of TRIAC with layer diagram.
  - (b) Explain the operation of step up chopper.
  - (c) Describe the operation of single phase full wave bridge converter with R-L load.



## ANSWER

**1(a)** Latching current - It is the minimum value of anode Current which it must attain during turn-on process to maintain conduction when gate signal is removed.


**1(b)**  $\frac{dV}{dt}$  Triggering - With forward voltage across the anode and cathode of an SCR, the two outer junctions  $J_1$  and  $J_3$  are forward biased, but inner junction  $J_2$  is reversed bias. This reverse biased junction  $J_2$  has the characteristic of a capacitor due to charges existing across the junction. If forward voltage is suddenly applied, a charging current through junction capacitance  $C_J$ , may turn on the SCR. Charging current

$$I_C = \frac{dQ}{dt} = \frac{dC_J V_a}{dt} = C_J \frac{dV_a}{dt}$$

Therefore, if the rise of the forward voltage is high, the charging current  $I_C$  would be more.

**1(c)** Delay Time ( $t_d$ ) - The delay time  $t_d$  is the time interval between the instant at which the gate current reaches  $0.9I_g$  and the instant at which anode current reaches  $0.1I_a$ . The delay time may also be defined as time during which anode voltage from  $V_a$  to  $0.9 V_a$ .

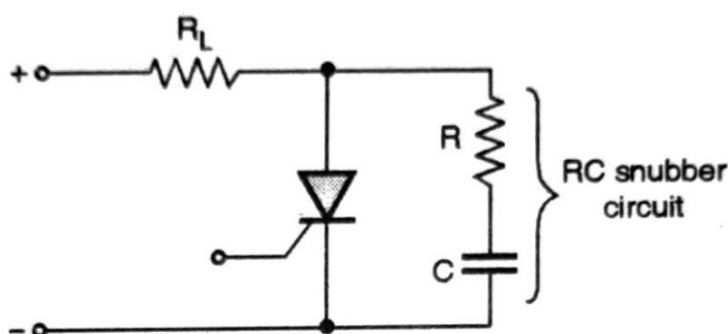**1(d) Snubber circuit** - A snubber circuit basically consists of a series - connected resistor and capacitor placed in shunt with an SCR.




**1(e)** Phase angle is the time interval between the instant the SCR is forward biased and the instant gate pulse is given to turn ON the SCR.

**1(f)** A chopper is a static device (or switch) used to obtain variable DC voltage from a source of constant DC voltage. Therefore, chopper may be thought of as DC equivalent of an AC transformer, since they behave in an identical manner

**1(g)** Duty cycle - It is the ratio of turn ON time to total time . It is denoted by  $\alpha$

$$\alpha = \frac{T_{ON}}{T} = \text{Duty cycle}$$


**2(a)** TRIAC - TRIAC is a four layer, six doped region and a three terminal device. Gate terminal is connected to both  $N_3$  and  $P_2$  so that gate triggers the device when both positive and negative voltage is applied. In the Same way  $MT_1$  is also connected to  $N_2$  and  $P_2$  regions and  $MT_2$  is connected to the  $P_1$  and  $N_4$  regions. So the polarity between the terminals decides the direction of the current through the layers.

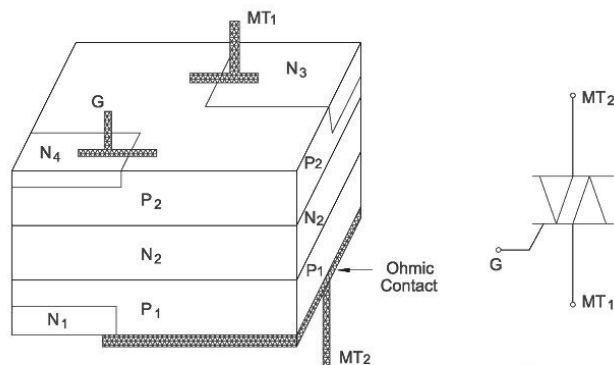
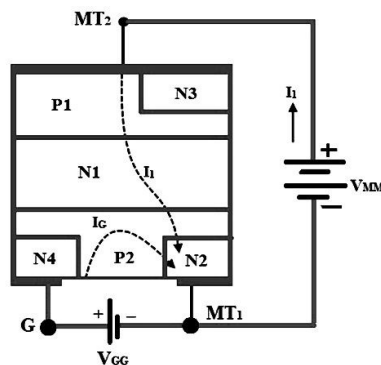
### Working of TRIAC:


There are four possible combinations of the potentials applied to the terminals.

Mode1:  $MT_2$  is positive and gate terminal is positive:




When the  $MT_2$  terminal is made positive with respect to the terminal  $MT_1$  and when positive voltage is applied at the gate terminal the path of the current flow from  $MT_2$  to  $MT_1$  will be  $P_1-N_1-P_2-N_2$ . The junction between  $P_1N_1$  and  $P_2N_2$  are forward biased and junction between  $N_1P_2$  is reverse biased and breakdown occurs at this junction.

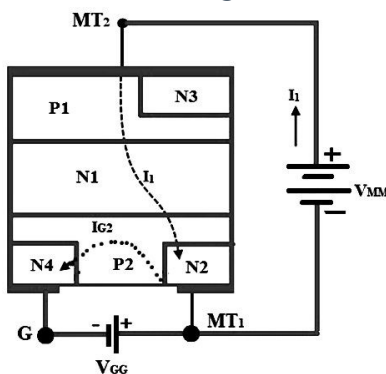Mode2:  $MT_2$  is positive and gate terminal is negative:




When the  $MT_2$  terminal is made positive with respect to the terminal  $MT_1$  and when negative voltage is applied at the gate terminal, initially the path of the current flow from  $MT_2$  to  $MT_1$  will be  $P_1-N_1-P_2-N_3$ . When the voltage applied at the  $MT_2$  terminal is further increased the junction  $P_2N_2$  is forward biased and the path of the current flow will be  $P_1-N_1-P_2-N_2$ . More Gate current is needed to turn the TRIAC.

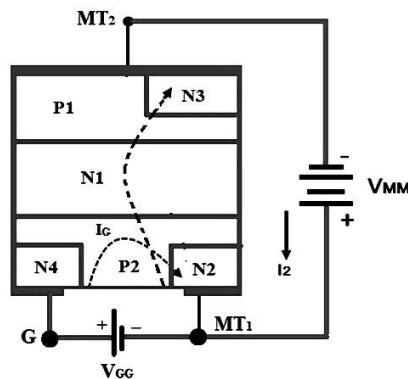Mode3:  $MT_2$  is negative and gate terminal is positive:




When the  $MT_2$  terminal is made positive with respect to the terminal  $MT_1$  and when negative voltage is applied at the gate terminal the path of the current flow from  $MT_2$  to  $MT_1$  will be  $P_2N_1P_1$ . The Junctions  $P_2N_1$  and  $P_1N_4$  are forward biased and the junction  $N_1P_1$  is reverse biased. So in this mode, TRIAC work in a negative biased region.

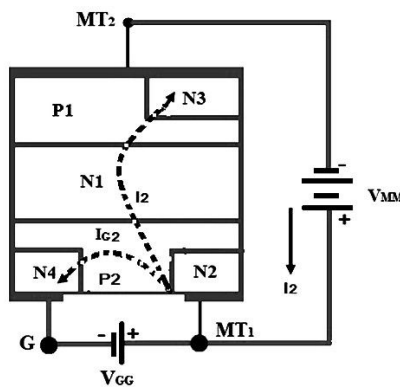Mode4:  $MT_2$  is negative and gate terminal is negative:



When the  $MT_2$  terminal is made negative with respect to the terminal  $MT_1$  and when negative voltage is applied at the gate terminal the path of the current flow from  $MT_2$  to  $MT_1$  will be  $P_2N_1P_1N_4$ .

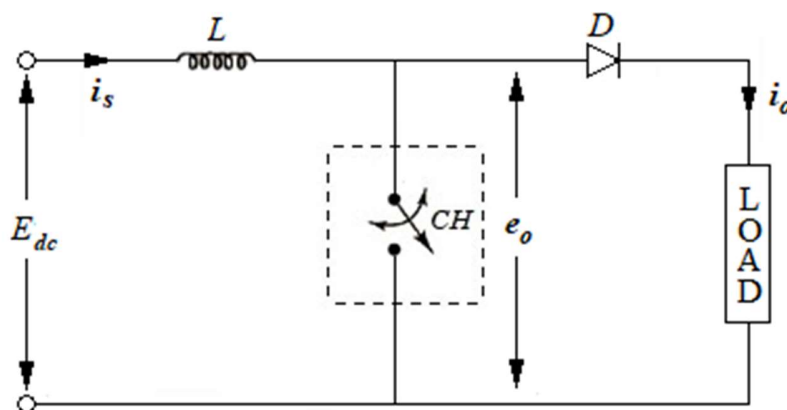**2(b)** Working principle of step-up CHOPPER:



When the chopper is ON, the inductor L is connected to the supply and stores energy during on period  $T_{ON}$ . When the chopper is made OFF, the inductor stored energy as well as Source  $E_{DC}$  supply the load. Hence the load voltage becomes

$$E_O = E_{DC} + L \frac{dI_{DC}}{dt}$$

During the time  $T_{ON}$  when chopper is ON, the energy input to the inductor from the source is given by  $W_I = E_{DC} I_{DC} T_{ON}$

During the time  $T_{OFF}$  when chopper is OFF, energy released by the inductor to the load is given by

$$W_O = (E_O - E_{DC}) I_{DC} T_{OFF}$$

Considering the system to be lossless, the above two energies will be equal.

Hence  $W_I = W_O$

$$\text{Or } E_{DC} I_{DC} T_{ON} = (E_O - E_{DC}) I_{DC} T_{OFF}$$

$$\text{Or } E_{DC} T_{ON} + E_{DC} T_{OFF} = E_O T_{OFF}$$

$$\text{Or } E_O = E_{DC} \frac{T_{ON} + T_{OFF}}{T_{OFF}}$$

$$\text{Or } E_O = E_{DC} \frac{T}{T_{OFF}}$$

$$\text{Or } E_O = E_{DC} \frac{1}{1 - \frac{T_{ON}}{T}}$$


$$\text{Or } E_O = \frac{E_{DC}}{1 - \alpha}$$

Hence the output voltage  $E_O$  will vary in the range  $E_{DC} < E_O < \infty$  for the variation of duty cycle  $\alpha$  in the range  $0 < \alpha < 1$ .
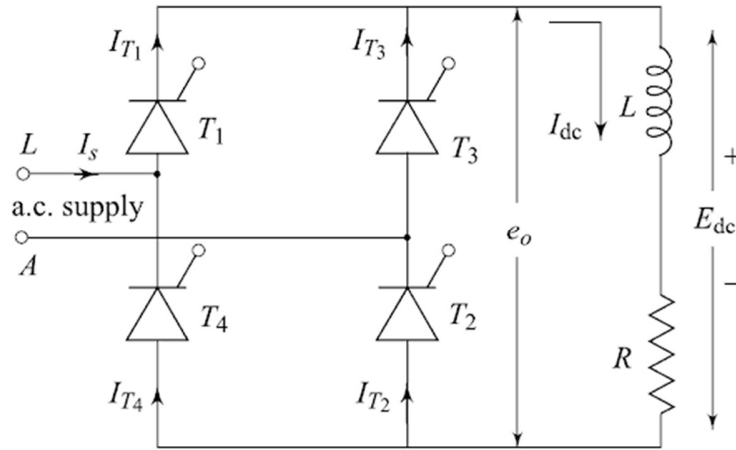
### 2(c) Operation of single phase full wave bridge converter with RL load:

During first positive half cycle, SCRs  $T_1$  and  $T_2$  are fired at firing angle  $\alpha$ . So the current flows through the path L- $T_1$ -L-R- $T_2$ -N. Supply voltage from this instant appears across output load terminal. At instant  $\pi$ , voltage reverses, however the current is maintained in the same direction which keeps the SCRs  $T_1$  and  $T_2$  conducting and hence the negative supply voltage appears across load terminals.

At an angle  $\pi + \alpha$ , SCRs  $T_3$  and  $T_4$  are fired. With this, the negative line voltage reverse-biases SCRs  $T_1$  and  $T_2$  to commute. Now the current flows through the path N- $T_3$ -L-R- $T_4$ -L. This continues in every half cycle and we get the output voltage across load.



The average load voltage is

$$E_{DC} = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} E_m \sin \omega t d(\omega t)$$

Or 
$$E_{DC} = \frac{E_m}{\pi} [-\cos \omega t]_{\pi}^{\pi+\alpha}$$

Or 
$$E_{DC} = \frac{2E_m}{\pi} \cos \alpha$$