

# PNS SCHOOL OF ENGINEERING & TECHNOLOGY

NISAMANI VIHAR, MARSHAGHAI, KENDRAPARA



DEPARTEMENT OF ELECTRONICS & TELECOMMUNICATION ENGINEERING

1ST INTERNAL ASSESSMENT EXAM QUESTIONS & ANSWER

SUB-DIGITAL ELECTRONICS (TH-3)

PREPARED BY :

ER. ADITYA NARAYAN JENA

LECTURER IN ETC

# **PNS School of Engineering & Technology**

Nishamani Vihar, Marshaghai, Kendrapara

**Internal Assessment Examination-2022(3rd Semester)**

**Subject : Th-3 -Digital Electronics**

**Branch : Computer Science & ETC Engineering**

Time : 1½ Hours

F.M. : 20

1. Answer all questions [2 x 5]

(a) What do you mean by base of a number system ?

(b) Convert  $(276)_8$  into  $(\quad)_{16}$  ?

(c) Find 2's Complement of  $(11.01)_2$ .

(d) Define min term and max term.

(e) Draw the gate symbol and truth table of 3 input NAND gate.

2. Answer any two questions. [5 x 2]

(a) State and prove De-Morgan's Theorem.

(b) Explain the working principle of full Adder with Truth Table and Logic Diagram.

(c) Solve by K-map :

$$F(A,B,C,D) = \Sigma m(1,3,7,11,15) + d(0, 2, 5)$$



### 1- (a) Base of a number system ÷

The number of digits used in a number system is known as base of that no. system.

For eg; The base of binary no. system is 2, since only 0 & 1 used in Binary number system.

(b)  $(276)_8$

$$= (010111110)_2$$

$$= (0000\ 1011\ 1110)_{16} = (0BE)_{16} \quad (\text{Ans})$$

(c)  $(11.01)_2$

$$1\text{'s complement} = 00.10$$

$$2\text{'s complement} = 00.10$$

---

$$+ 1$$

$$(00.11) = (00.11)_2 \quad (\text{Ans})$$

(d) Min term ÷


In SOP expression, the term which contains all the variables in direct or complement form, is known as min term.

Max term ÷

In POS expression, the term which contains all the variable in direct or complement form, is known as max term.

(e) 3 input NAND gate ÷

Gate symbol -

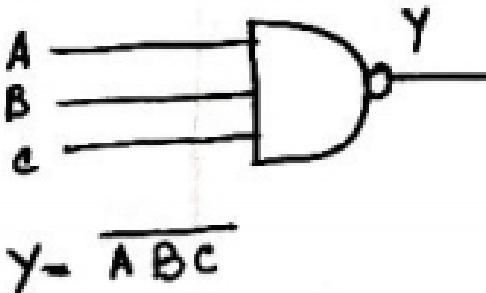

Truth table -

Input			Output
A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

2- (a) Demorgan's Theorem ÷

$$(I) \quad \overline{X+Y} = \overline{X} \cdot \overline{Y}$$

$$(II) \quad \overline{X \cdot Y} = \overline{X} + \overline{Y}$$

Where x , y are two logic variables

proof

$$(i) \quad \overline{X+Y} = \overline{X} \cdot \overline{Y}$$

Truth table ÷

X	Y	X+Y	$\overline{X+Y}$	$\overline{X}$	$\overline{Y}$	$\overline{X} \cdot \overline{Y}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

From truth table  $\overline{X+Y} = \overline{X} \cdot \overline{Y}$  (Proved)

$$(ii) \quad \overline{X \cdot Y} = \overline{X} + \overline{Y}$$

Truth table ÷

X	Y	X.Y	$\overline{X.Y}$	$\overline{X}$	$\overline{Y}$	$\overline{X+Y}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

From truth table,  $\overline{X.Y} = \overline{X} + \overline{Y}$  (Proved)

2 (b)

FULL ADDER ÷

It is a combinational logic circuit which perform the arithmetic addition of only 3 binary bits.

- Here no of inputs = 3 i.e x,y and z; and no of output = 2 i.e s,c

Where S = Sum

C = Carry



<BD of a full adder>

Truth Table ÷

Input			Output	
x	y	z	s	c
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Expression for s ÷

x \ yz	00	01	11	10
0		1		1
1	1		1	

$$S = \bar{x} \bar{y} z + \bar{x} y \bar{z} + x \bar{y} \bar{z} + x y z$$

$$= \bar{x} (\bar{y} z + y \bar{z}) + x (\bar{y} \bar{z} + y z)$$

Let

$$\bar{y} z + y \bar{z} = A$$

$$\bar{A} = \bar{y} \bar{z} + y z$$

$$S = \bar{X} A + X \bar{A}$$

$$= x \oplus A$$

$$= x \oplus (\bar{y} z + y \bar{z})$$

$$= x \oplus y \oplus z$$

Expression for c ÷

x \ yz	00	01	11	10
0	00	01	1	10
1		1	1	1


$$C = y z + x z + y x$$

$$= x y + y z + x z$$

Logic diagram of full odder ÷

$$S = x \oplus y \oplus z$$

$$C = xy + yz + xz$$

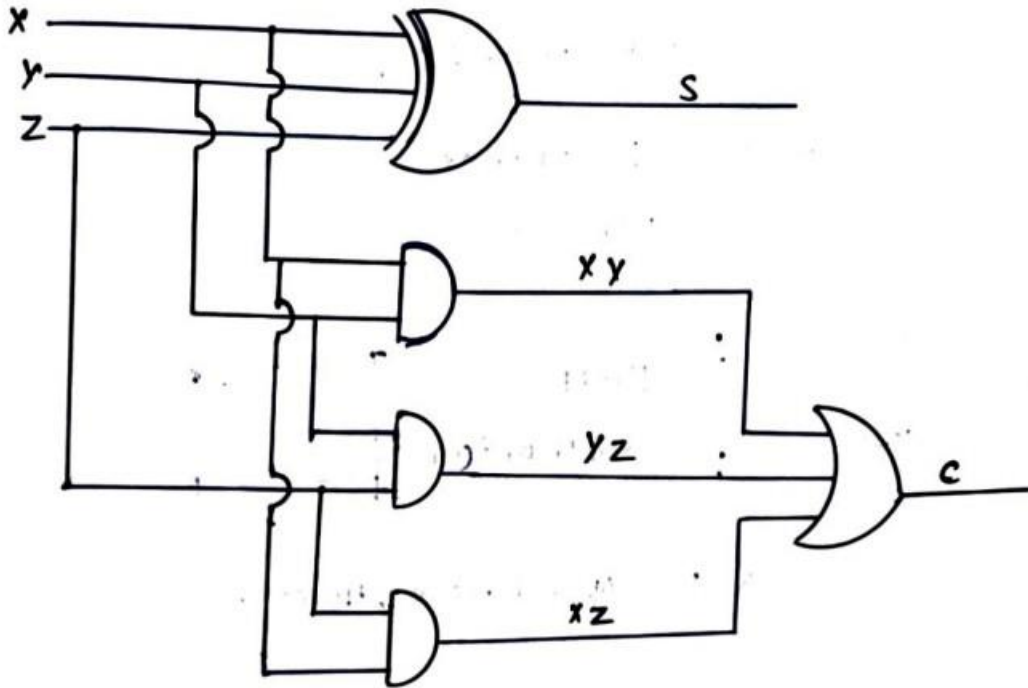

2- (C) Solve by k-map

$$F(A, B, C, D) = \sum m(1, 3, 7, 11, 15) + d(0, 2, 5)$$

AB \ CD	00	01	11	10
00	x	1	1	x
01		x	1	
11			1	
10			1	

$$F = \overline{A} \overline{B} + CD$$

(ans)