

# PNS SCHOOL OF ENGINEERING AND TECHNOLOGY

NISAMANI VIHAR, MARSHAGHAI, KENDRAPARA



DEPARTMENT OF ELECTRONICS & TELECOMMUNICATION ENGINEERING

1<sup>ST</sup> INTERNAL ASSESSMENT EXAM QUESTIONS & ANSWER

SUB- DIGITAL ELECTRONICS AND MICROPROCESSOR (TH-3)

PREPARED BY :

ER.ADITYA NARAYA JENA

LECTURER IN ETC

# **PNS School of Engineering & Technology**

Nishamani Vihar, Marshaghai, Kendrapara

**Internal Assessment Examination-2022(5th Semester)**

**Subject : Th-3 -Digital Electronics & Microprocessor**

**Branch : Electrical Engineering**

Time :  $1\frac{1}{2}$  Hours

F.M. : 20

1. Answer all questions [2 x 5]
  - (a) What do you mean Radix of a no system ?
  - (b) Convert  $(475)_{10}$  into  $(\quad)_{2}$  ?
  - (c) Find XS-3 Code of 897.
  - (d) Define Don't Care Condition.
  - (e) Draw the gate symbol and truth table of 3 input NOR gate.
  
2. Answer any two questions. [5 x 2]
  - (a) State and prove De-Morgan's Theorem.
  - (b) Explain the working principle of full subtractor with Truth Table and Logic Diagram.
  - (c) Solve by K-map :  
$$F(A,B,C,D) = \Sigma m(0,5,6,15) + d(2,3,7,10,11,13)$$



1- (a) Radix ÷

The number of digits used in a number system , is called radix of the number system.

For eg; binary number system only 0 and 1 are used . so radix is 2.

(b)  $(478)_{10}$ ;

$$\begin{array}{r}
 2 \mid 475 \\
 \hline
 2 \mid 237 - 1 \\
 \hline
 2 \mid 118 - 1 \\
 \hline
 2 \mid 59 - 0 \\
 \hline
 2 \mid 29 - 1 \\
 \hline
 2 \mid 14 - 1 \\
 \hline
 2 \mid 7 - 0 \\
 \hline
 2 \mid 3 - 1 \\
 \hline
 2 \mid 1 - 1 \\
 \hline
 0 - 1
 \end{array}$$

$$=(1110111011)_2 \quad (\text{ANS})$$

(c) XS-3 code of 897= 8 9 7

$$+3 3 3$$

---


$$11 12 10$$


$$=(1011 1100 1010) \quad (\text{Ans})$$

(d) Don't care condition ÷

The combinations which are never occur in the outputs, is known as don't care condition.

For eg; in decimal no. system (10-15) are don't care conditions.

(e) 3 input NOR gate ÷

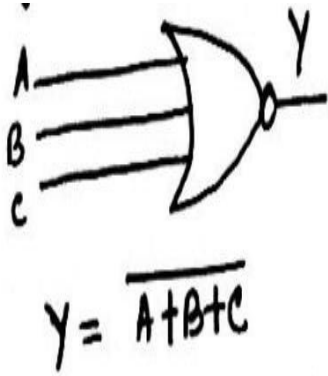

Truth table ÷

Input			Output
A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

2-(a) Demorgan's Theorem ÷

(I)  $\overline{X+Y} = \overline{X} \cdot \overline{Y}$

(II)  $\overline{X \cdot Y} = \overline{X} + \overline{Y}$

Where x , y are two logic variables

proof

(i)  $\overline{X+Y} = \overline{X} \cdot \overline{Y}$

Truth table ÷

X	Y	X+Y	$\overline{X+Y}$	$\overline{X}$	$\overline{Y}$	$\overline{X} \cdot \overline{Y}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

From truth table  $\overline{X+Y} = \overline{X} \cdot \overline{Y}$

(ii)  $\overline{X \cdot Y} = \overline{X} + \overline{Y}$

Truth table ÷

X	Y	X.Y	$\overline{X \cdot Y}$	$\overline{X}$	$\overline{Y}$	$\overline{X} + \overline{Y}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

From truth table,  $\overline{X \cdot Y} = \overline{X} + \overline{Y}$  (Proved)

2- (b) Full subtractor ÷


It is a combinational logic circuit which performs the arithmetic Substraction of 3 binary bits.

Here no of input =3 i.e x, y, z; and no of outputs =2i.e D and B

Where

D = difference

B = borrow

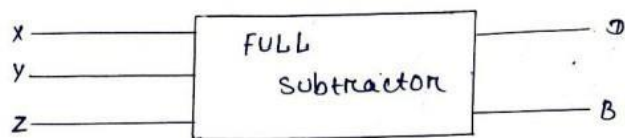

<BD of a full subtractor>

Truth table ÷

Inputs			outputs	
X	Y	Y	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Expression for D:

Y z	00	01	11	10
X		1		1
0		1		1
1	1		1	

$$D = \overline{x} \overline{y} z + \overline{x} y \overline{z} + x \overline{y} \overline{z} + x y z$$

$$= \overline{x} (\overline{y} z + y \overline{z}) + x (\overline{y} \overline{z} + y z)$$

$$\text{Let } A = \overline{y} z + y \overline{z}$$

$$\overline{A} = \overline{y} \overline{z} + y z$$

$$D = \overline{X} A + X \overline{A}$$

$$= X \oplus A$$

$$= X \oplus (\overline{y} z + y \overline{z})$$

$$= x \oplus y \oplus z$$

Expression for B:


Y z	00	01	11	10
X		1	1	1
0		1	1	1
1			1	

$$B = \overline{x} z + \overline{x} y + y z$$

Logic diagram of full subtractor ÷

$$D = x \oplus y \oplus z$$

$$B = \bar{x}y + \bar{x}z + yz$$

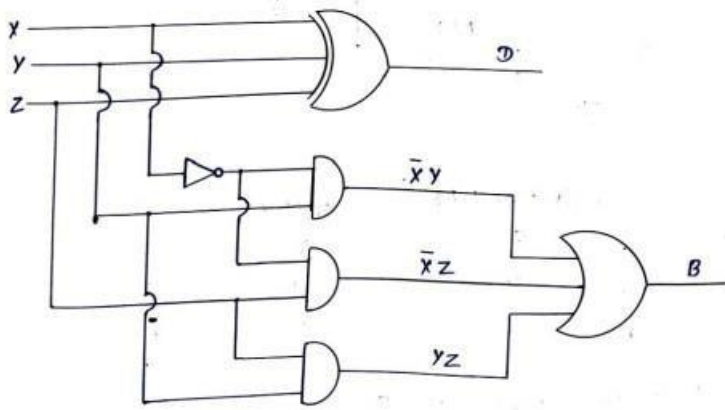

2 (c) solve by k-map

$$F(A, B, C, D) = \sum m(5, 0, 6, 15) + d(2, 3, 7, 10, 11, 13)$$

AB \ CD	00	01	11	10
00	1		x	x
01		1	x	1
11		x	1	
10			x	x

$$F = BD + \bar{A}C + \bar{A}\bar{B}\bar{D}$$